

# Lab 7 – Counters/Dividers

*Name:* Von Kaukeano

*Date:* 10/23/18

*Course:* Digital Circuit Design Lab – ECE 2613

*Section #:* 001

## Summary/Abstract

The lab consisted of two different modules, a parameterized module which was the divider and the ir emitter module. The divider module takes an input and counts from  $n$  to 0 and will output an impulse at  $t_c$  being 1 when count is 0, thus dividing the 100Mhz internal clock by  $n + 1$ . The second module is a series of instantiations of the divider module with four implementations using the same divider design, but different BIT\_SIZE parameters to create the required 38 kHz signal. After instantiating them an AND gate combined the signals creating the output signal emitter out.

## Introduction

In this lab we designed circuit that will modulate a signal to drive an IR emitter with characteristics that match a particular IR receiver module. We created a design to create signals with two frequencies which are a carrier and a modulation frequency. The carrier frequency is the fundamental frequency and the modulation frequency defines how this carrier wave is turned on and off. In our design the signals with these two frequencies are logically AND'ed and resultant output appears to be bursts of carrier frequency signals with the burst frequency being the modulation frequency.

## Procedure

We designed two separate modules. The divider module which we learned how to design in class. For the second module, the first instance was designed to generate a 76 kHz pulse train. The signal from the first will connect to the enable input of another divider to create a square wave by dividing by 2. The third created the 10 cycles on and 10 cycles off modulation. The final divider generates the modulation square wave signal by toggling from high to low for groups of 10 cycles. After creating these modules, we AND gated the outputs to create a final output emitter out.

# Results

## Design Code

```
//  
// lab7 : version 10/15/2018  
//  
module divider #(parameter BIT_SIZE=4)  
  (output logic tc, output logic [BIT_SIZE-1:0] count, input logic clk,  
   input logic rst, input logic ena, input logic [BIT_SIZE-1:0] init_count);  
  
  logic [BIT_SIZE-1:0] next_count;  
  
  // enter your code here  
  
always_ff @ (posedge clk) begin  
  count <= next_count;  
end  
  
always_comb begin  
  
  tc = 0;  
  next_count = count;  
  
  if (ena == 1) begin  
    next_count = count - 1;  
    if (count == 0) begin  
      tc = 1;  
      next_count = init_count;  
    end  
  end  
  
  if (rst == 1) begin  
    next_count = init_count;  
  end  
end  
endmodule
```

```
//  
// lab7 : version 10/15/2018  
//  
module ir_emitter (output logic emitter_out, input logic clk, input logic rst, input logic ena);  
  
  logic tc_carrier, tc_carrier_2, tc_modulator;  
  logic sw_carrier, sw_modulator;  
  
  // enter your code here - declare internal signals  
  
  // carrier divide by 100MHz/38kHz / 2 = 1315 (rounded up)  
  // enter your code here  
  divider #(BIT_SIZE(11)) u1 (.tc(tc_carrier_2), .count(), .clk(clk), .rst(rst), .ena(ena), .init_count(11'd1315));  
  // carrier divide by 2 to make it a square wave of 50% duty cycle  
  // enter your code here  
  divider #(BIT_SIZE(1)) u2 (.tc(tc_carrier), .count(sw_carrier), .clk(clk), .rst(rst), .ena(tc_carrier_2), .init_count(1));  
  
  // modulation divide by 10 (10 on ... 10 off)  
  // enter your code here  
  divider #(BIT_SIZE(4)) u3 (.tc(tc_modulator), .count(), .clk(clk), .rst(rst), .ena(tc_carrier), .init_count(9));  
  
  // modulation divide by 2 to make it a square wave of 50% duty cycle  
  // enter your code here  
  divider #(BIT_SIZE(1)) u4 (.tc(tc), .count(sw_modulator), .clk(clk), .rst(rst), .ena(tc_modulator), .init_count(1));  
  
  // AND gate to create the emitter out signal  
  // enter your code here  
  
  assign emitter_out = sw_carrier & sw_modulator;  
  
endmodule
```

## Simulation Results

```
source tb_divider.tcl
## run 1000ns
Testing divide by 10 - view and analyze timing diagram.
Time for tc going low: 0.000000 nsec
Time for tc going high: 95.000000 nsec
Time for tc going low: 105.000000 nsec
Time for tc going high: 195.000000 nsec
Time for tc going low: 205.000000 nsec
Time for tc going high: 295.000000 nsec
Time for tc going low: 305.000000 nsec
Time for tc going high: 395.000000 nsec
Time for tc going low: 400.000000 nsec
Time for tc going high: 500.000000 nsec
Time for tc going low: 505.000000 nsec
Time for tc going high: 595.000000 nsec
Time for tc going low: 605.000000 nsec
Time for tc going high: 695.000000 nsec
Time for tc going low: 705.000000 nsec
Time for tc going high: 795.000000 nsec
Time for tc going low: 805.000000 nsec
Time for tc going high: 895.000000 nsec
Simulation complete!!!
$finish called at time : 900 ns : File "/home/tuh42003/2613_2018f/lab7/tb_divider.sv" Line
49
## exit
INFO: [Common 17-206] Exiting xsim at Tue Oct 16 14:07:31 2018...
Compressing vcd file to lxt2 file. ...
```

```
source tb_divider.tcl
## run 1000ns
Testing divide by 10 - view and analyze timing diagram.
Time for tc going low: 0.000000 nsec
Time for tc going high: 95.000000 nsec
Time for tc going low: 105.000000 nsec
Time for tc going high: 195.000000 nsec
Time for tc going low: 205.000000 nsec
Time for tc going high: 295.000000 nsec
Time for tc going low: 305.000000 nsec
Time for tc going high: 395.000000 nsec
Time for tc going low: 400.000000 nsec
Time for tc going high: 500.000000 nsec
Time for tc going low: 505.000000 nsec
Time for tc going high: 595.000000 nsec
Time for tc going low: 605.000000 nsec
Time for tc going high: 695.000000 nsec
Time for tc going low: 705.000000 nsec
Time for tc going high: 795.000000 nsec
Time for tc going low: 805.000000 nsec
Time for tc going high: 895.000000 nsec
Simulation complete!!!
$finish called at time : 900 ns : File "/home/tuh42003/2613_2018f/lab7/tb_divider.sv" Line
49
## exit
INFO: [Common 17-206] Exiting xsim at Tue Oct 16 14:07:31 2018...
Compressing vcd file to lxt2 file. ...
```

## Hardware Implementation

*My design was demonstrated to Catherine on the afternoon of 10/16 during the lab period.*

## Conclusion

After creating both the divider and then instantiating them we used the gtkwave application which was visually appealing for understand the clock cycles and what happens at ever cycle. This lab was the most interesting, but one of the hardest to understand. At the end the final signal was shown along with the two signal that we AND'ed.

## Appendix

